Introduction to Electric Circuits (1	0 minutes)
Read the following text and answer the	e questions:
	nodern technology, powering everything from smartphones to ork is essential for any aspiring scientist, engineer, or inventor.
1. What is the primary function of a	a battery in an electric circuit?
2. Why is understanding electric ci	rcuits important?
Understanding Circuit Componen	ts (15 minutes)
Match the following circuit component	s with their descriptions:
Component	Description
Battery	
Wires	

Devices

Switch

Building a Simple Electric Circuit (20 minutes)	
Follow these steps to build a simple electric circuit:	
 Connect the battery to the wires. Connect the wires to the device (e.g., light bulb). Add a switch to control the flow of electricity. 	

Series and Parallel Circuits (20 minutes)

Build a series circuit and a parallel circuit using two light bulbs and a battery. What are the differences between the two circuits?

Circuit Type	Description
Series Circuit	
Parallel Circuit	

Circuit	Safety (15 minutes)
Read th	ne following safety guidelines and answer the questions:
	vorking with electric circuits, safety is crucial: Always handle electrical components with care. short circuits. Keep electrical components away from water.
1. W	/hy is it important to handle electrical components with care?
2. V	/hat can happen if you touch a short circuit?
Desigr	ning and Building a Circuit (25 minutes)
Design	ning and Building a Circuit (25 minutes) and build a circuit that powers a small device (e.g., a buzzer). What components do you need, and ll you connect them?
Design how wi	and build a circuit that powers a small device (e.g., a buzzer). What components do you need, and ll you connect them?
Design how wi	and build a circuit that powers a small device (e.g., a buzzer). What components do you need, and ll you connect them?
Design how wi	and build a circuit that powers a small device (e.g., a buzzer). What components do you need, and ll you connect them?
Design how wi	and build a circuit that powers a small device (e.g., a buzzer). What components do you need, and ll you connect them?
Design how wi	and build a circuit that powers a small device (e.g., a buzzer). What components do you need, and ll you connect them?
Design how win	and build a circuit that powers a small device (e.g., a buzzer). What components do you need, and ll you connect them? idual Reflection: What components do you need for your circuit?
Design how win	and build a circuit that powers a small device (e.g., a buzzer). What components do you need, and ll you connect them?
Design how win	and build a circuit that powers a small device (e.g., a buzzer). What components do you need, and ll you connect them? idual Reflection: What components do you need for your circuit?
Design how win	and build a circuit that powers a small device (e.g., a buzzer). What components do you need, and ll you connect them? idual Reflection: What components do you need for your circuit?

Differentiated A	ctivities for Mixed-Ability Groups (20 minutes)
Choose one of the	following activities:
1. For strug 2. For advar	gling students: Identify circuit components and their functions. nced students: Design and build a complex circuit with multiple components.
[Space for ac	tivity]
Conclusion (10	minutes)
Reflect on what yo	ou have learned about electric circuits:
Individual Refle	vetion: you learn about electric circuits?

Page 1 of 4

2. How can you apply what you learned in real-life situations?